



Лекция 2.


Основные концепции и инструменты


План лекции


- Обобщенная структура процессора
- Классификация цифровых интегральных схем
- Программируемая логическая интегральная схема (FPGA)
- Основы языка описания аппаратуры Verilog HDL
- Критический путь


Машина с хранимой в памяти программой

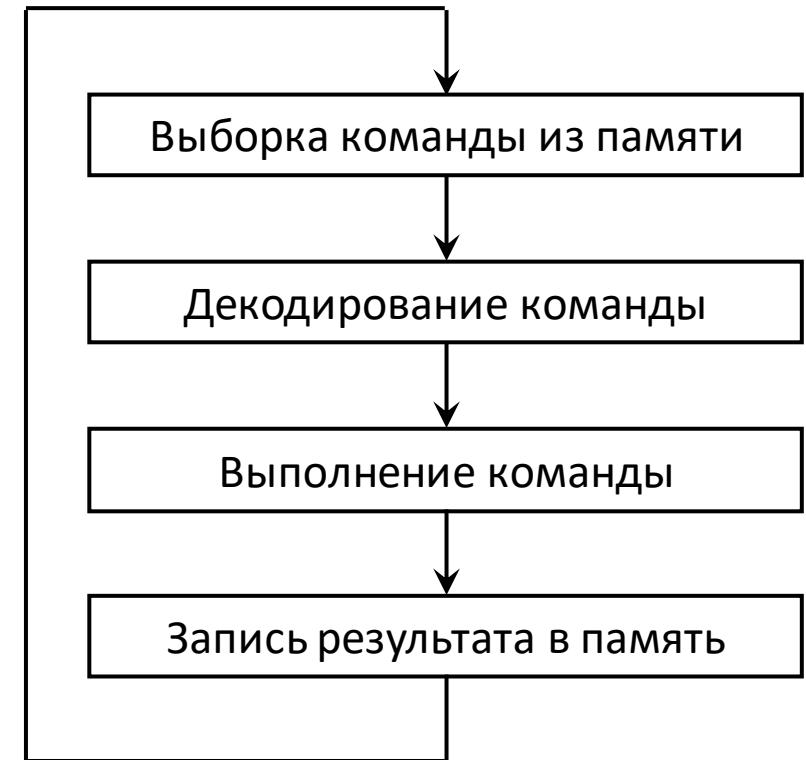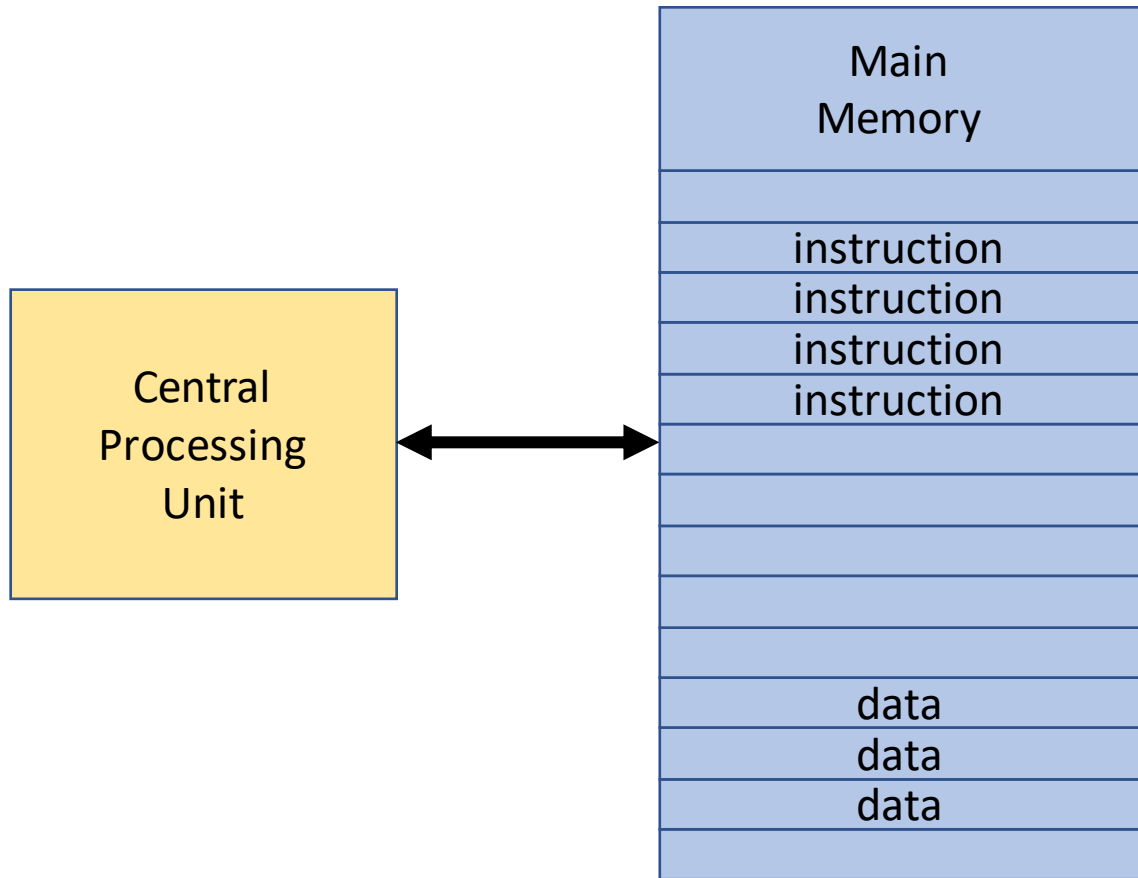


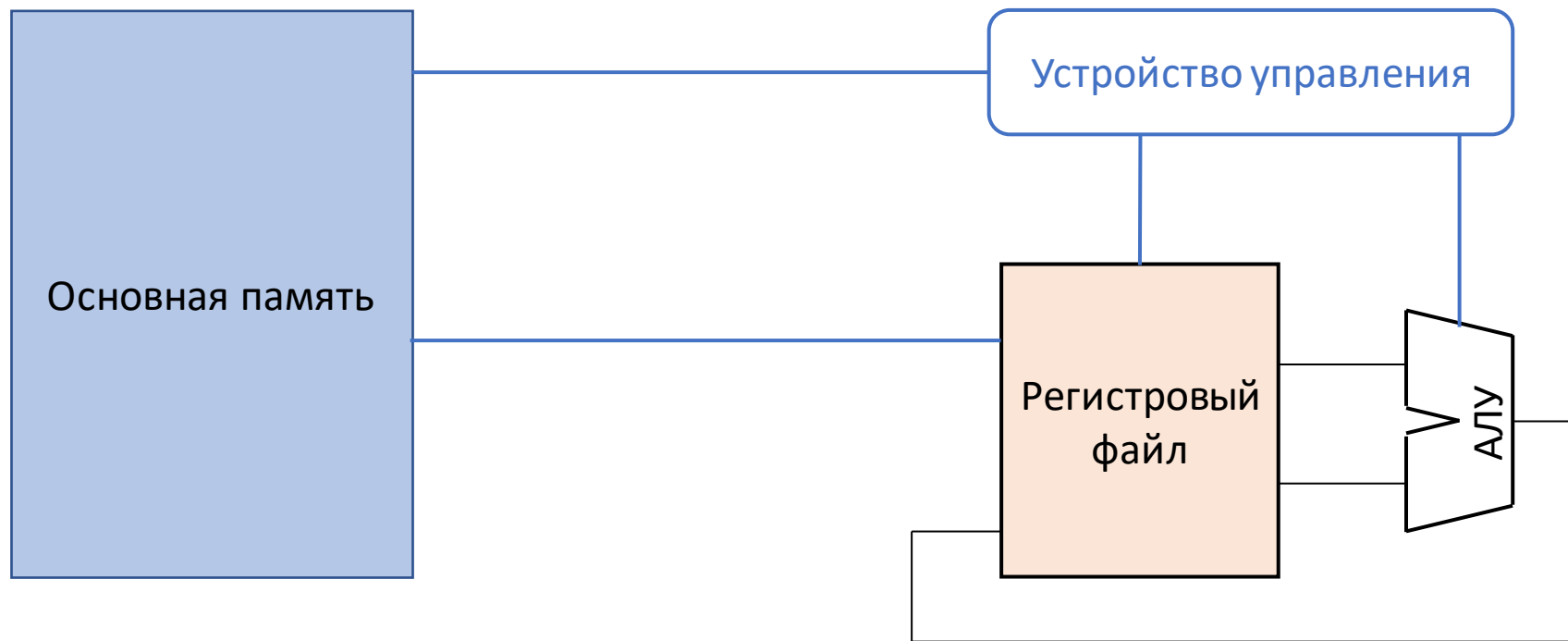


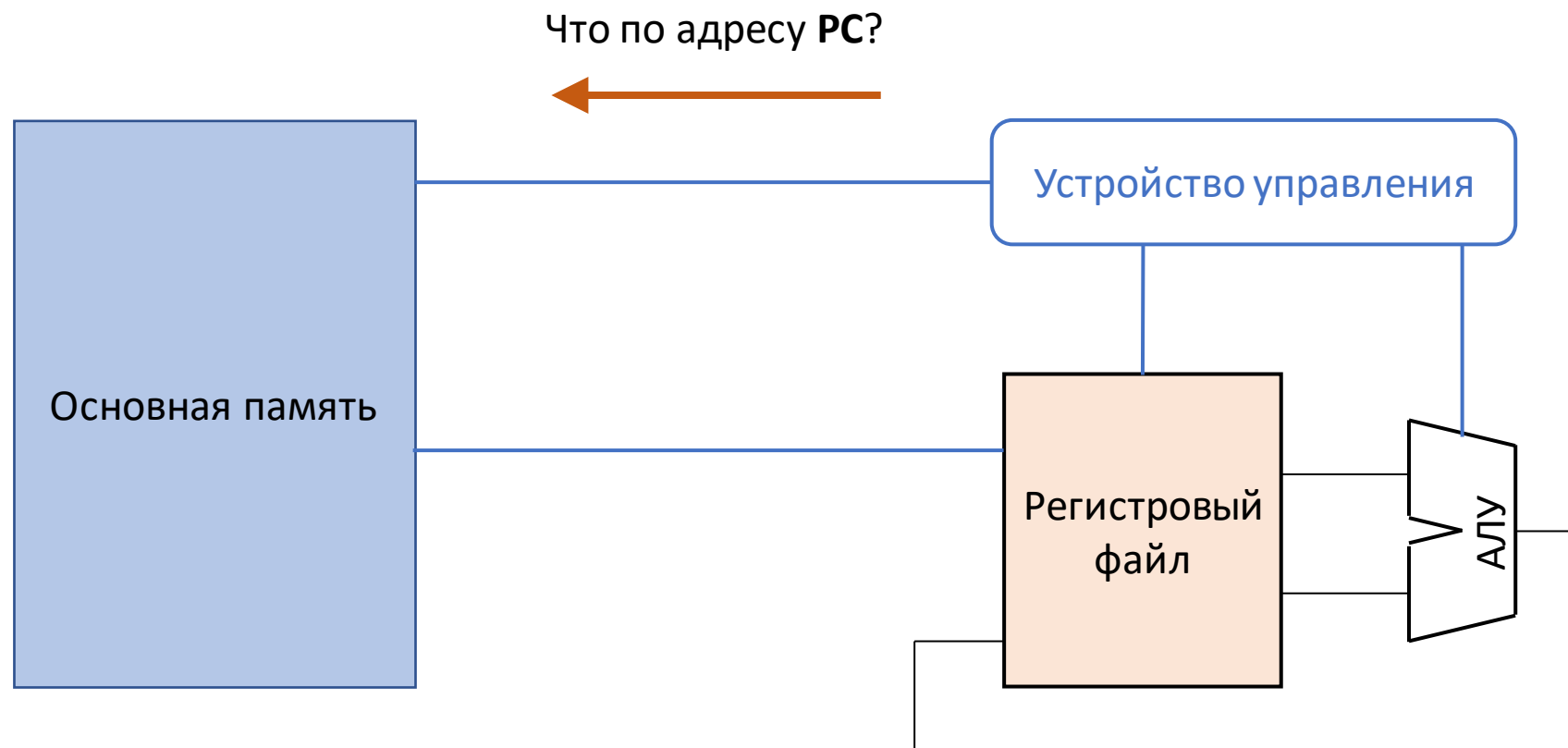


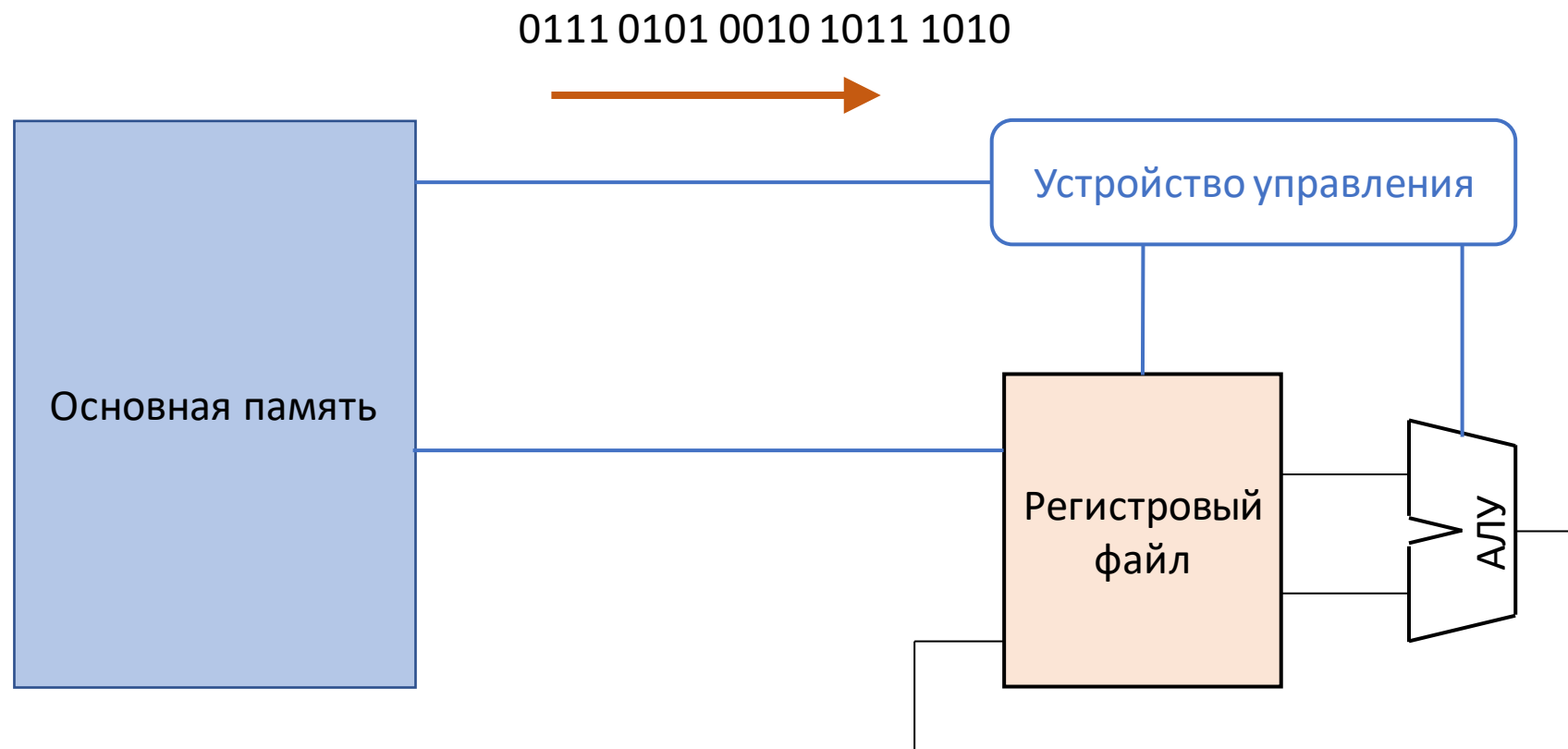


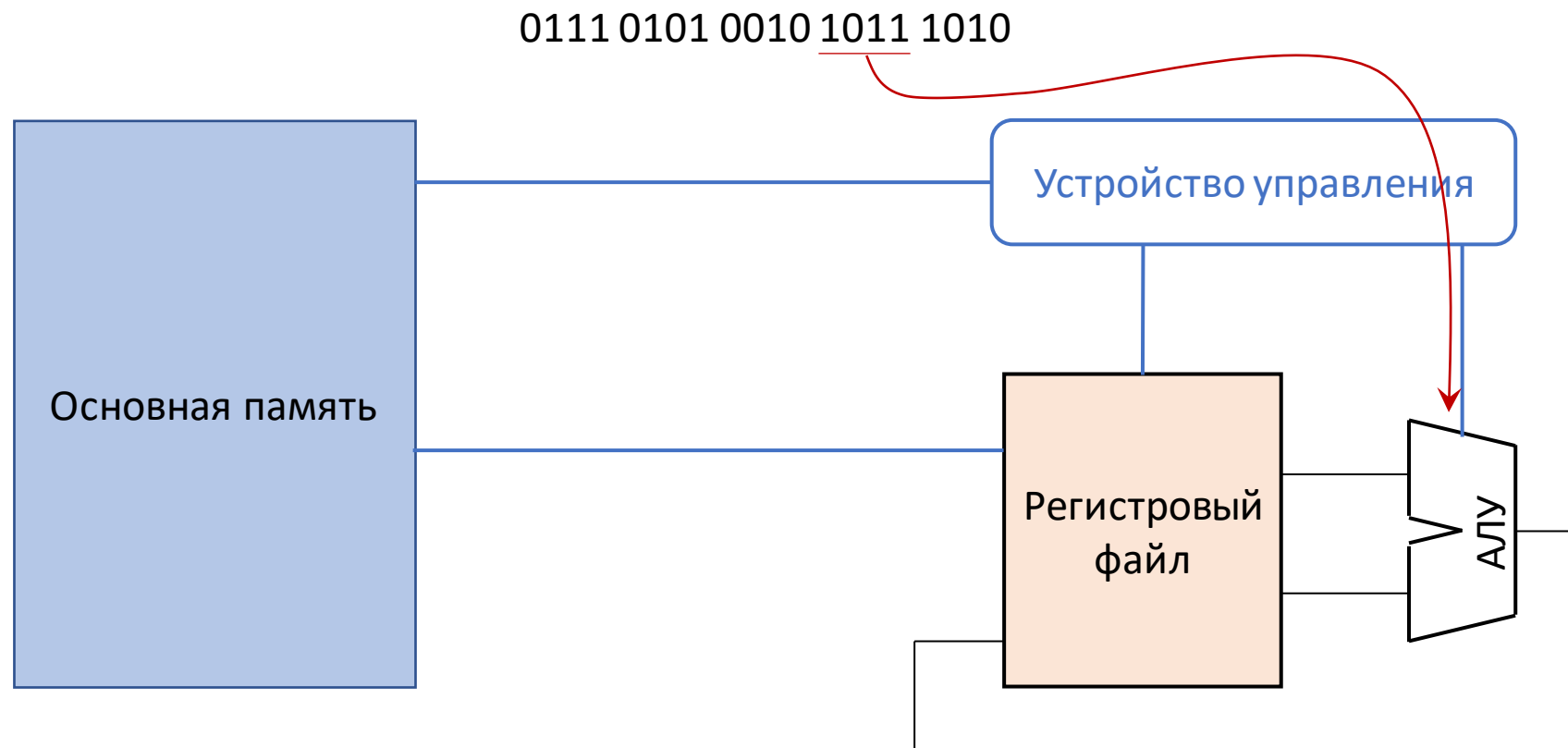


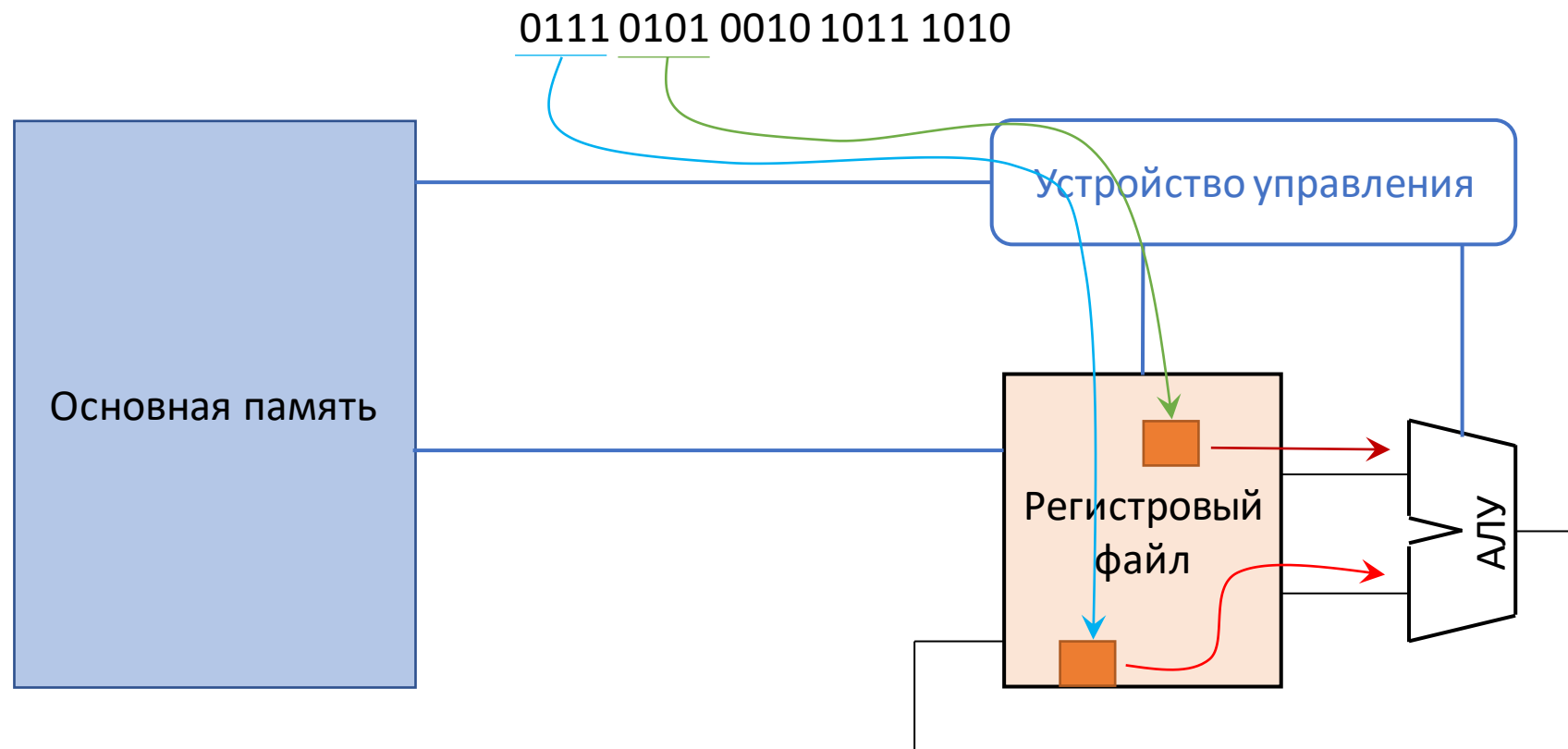


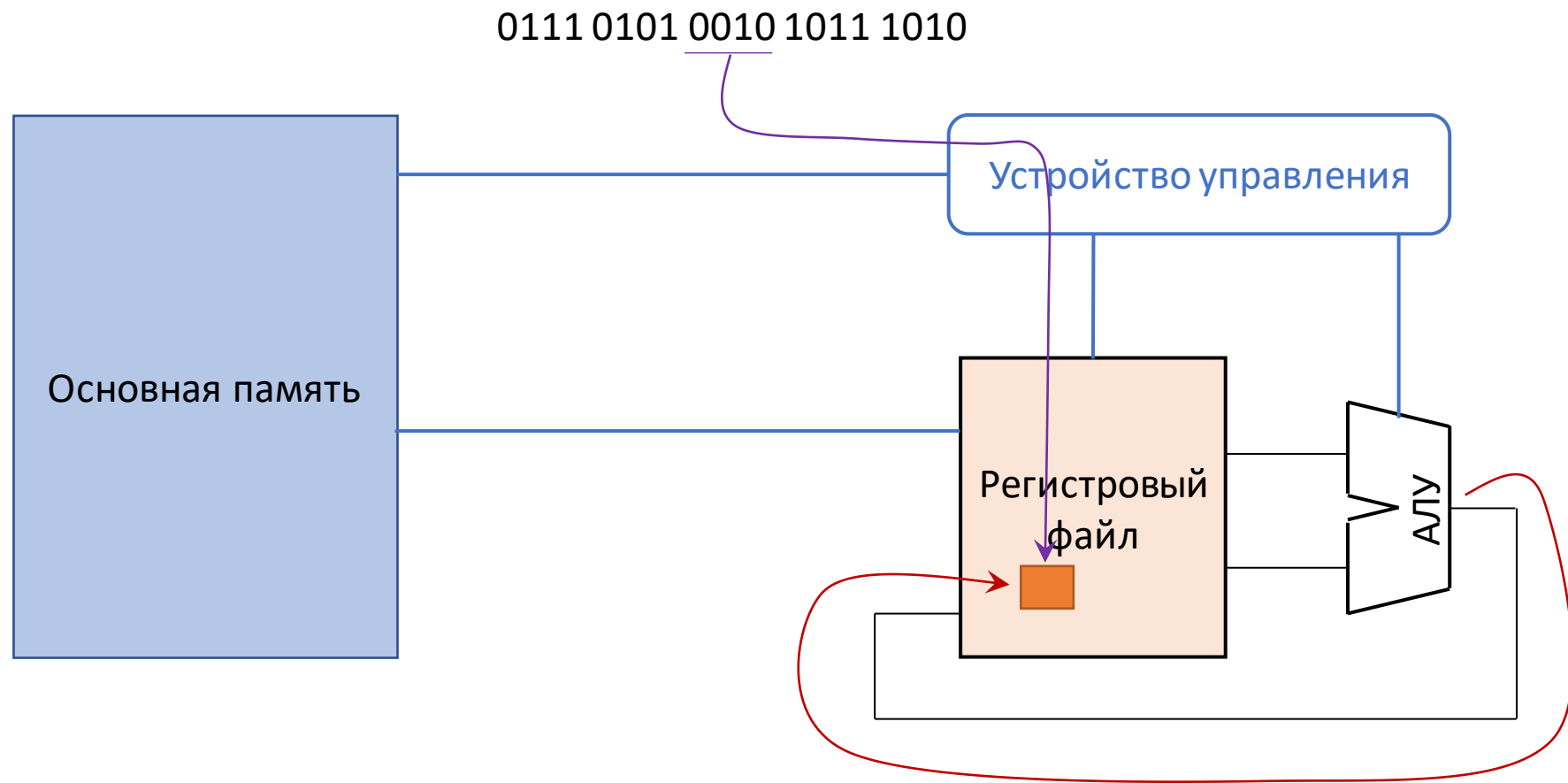

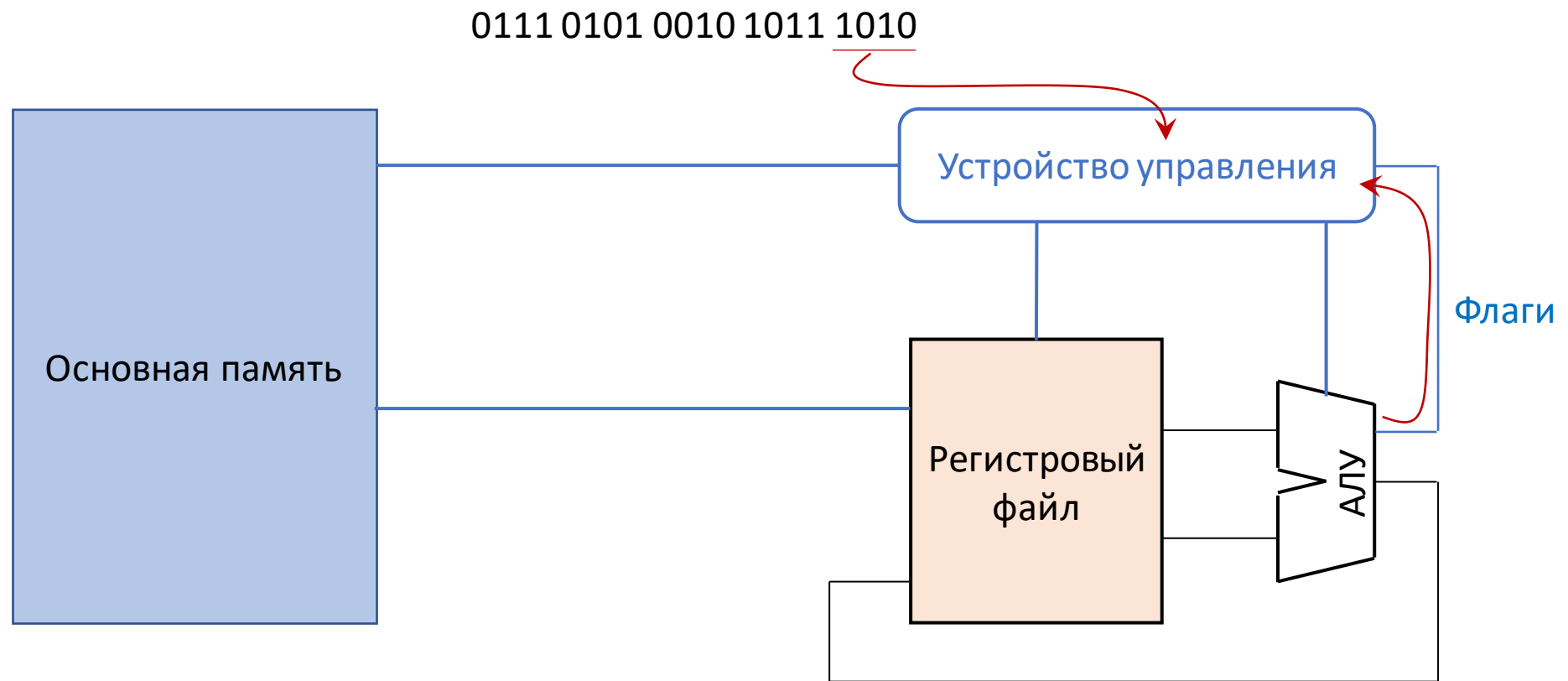


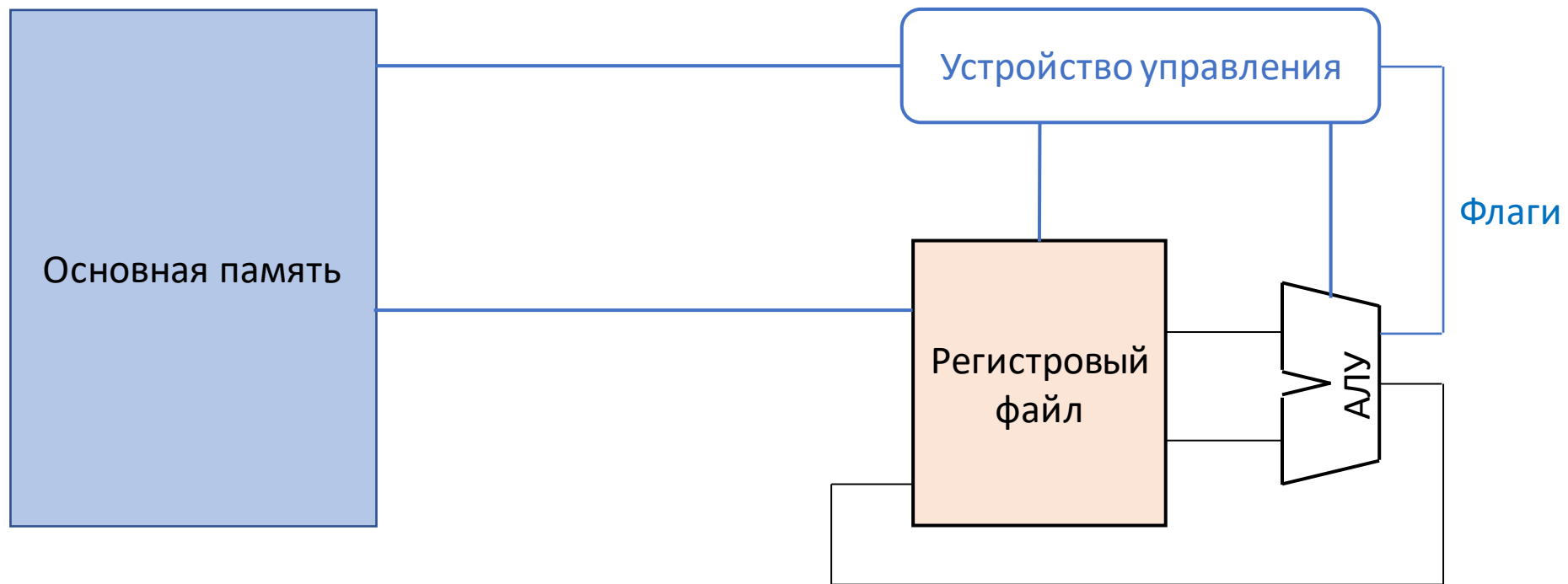


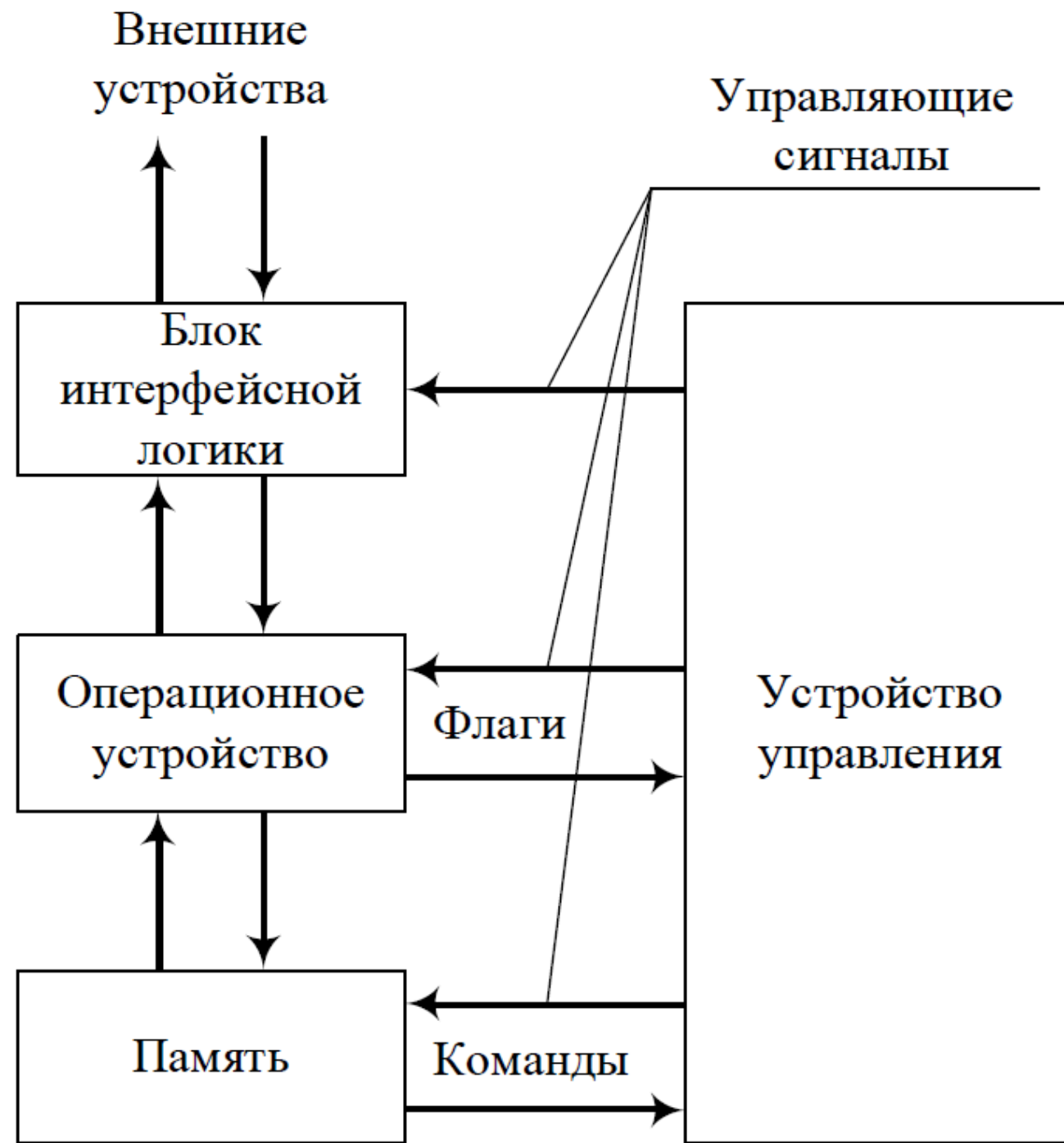


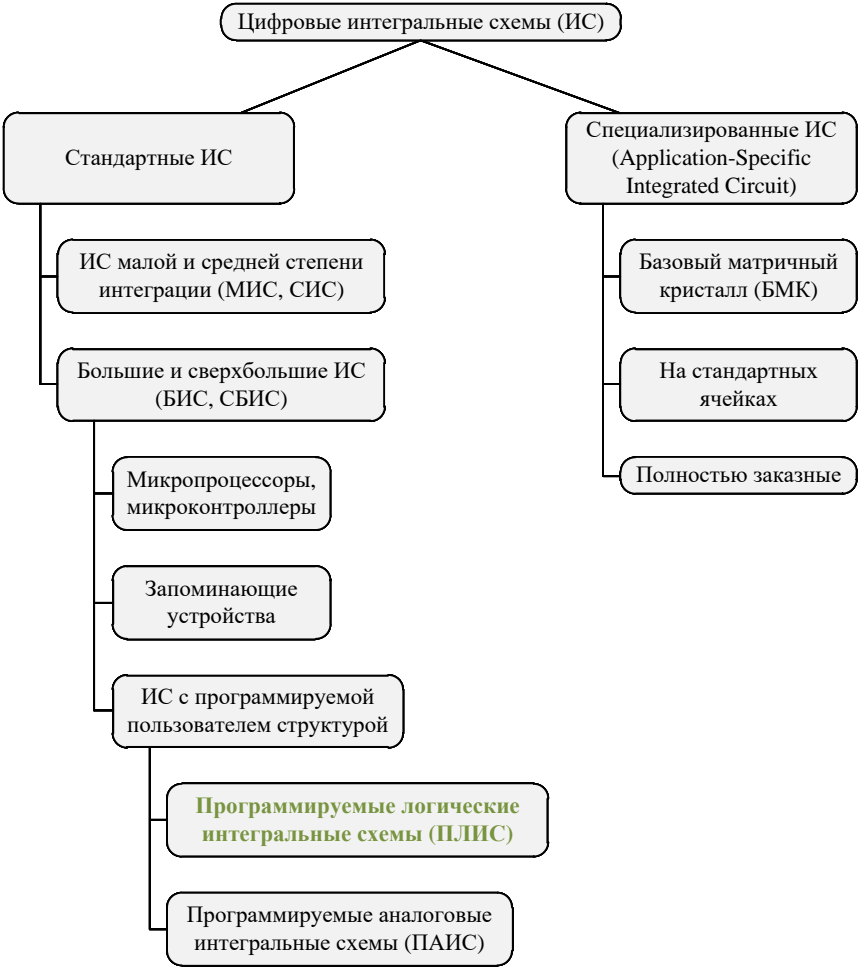



FPGA

 



Мультиплексор

  



Мультиплексор

  



Мультиплексор

  



Мультиплексор

  



Мультиплексор

  




Мультиплексор

  


Мультиплексор

  


Мультиплексор

 
 
 



LE

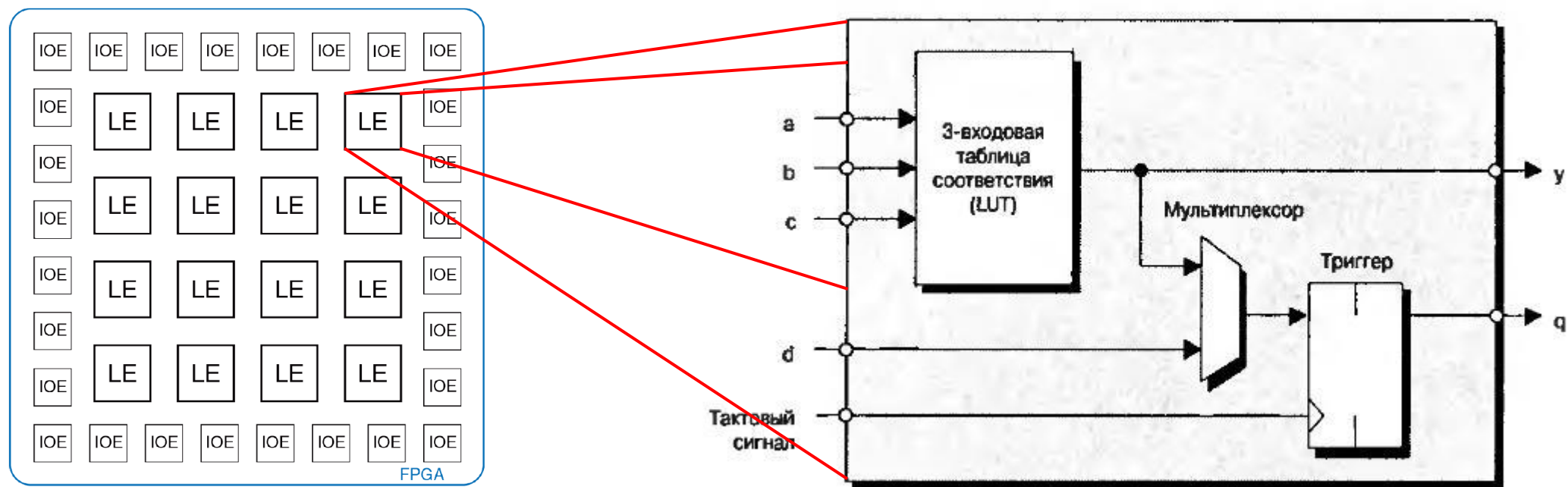



LE

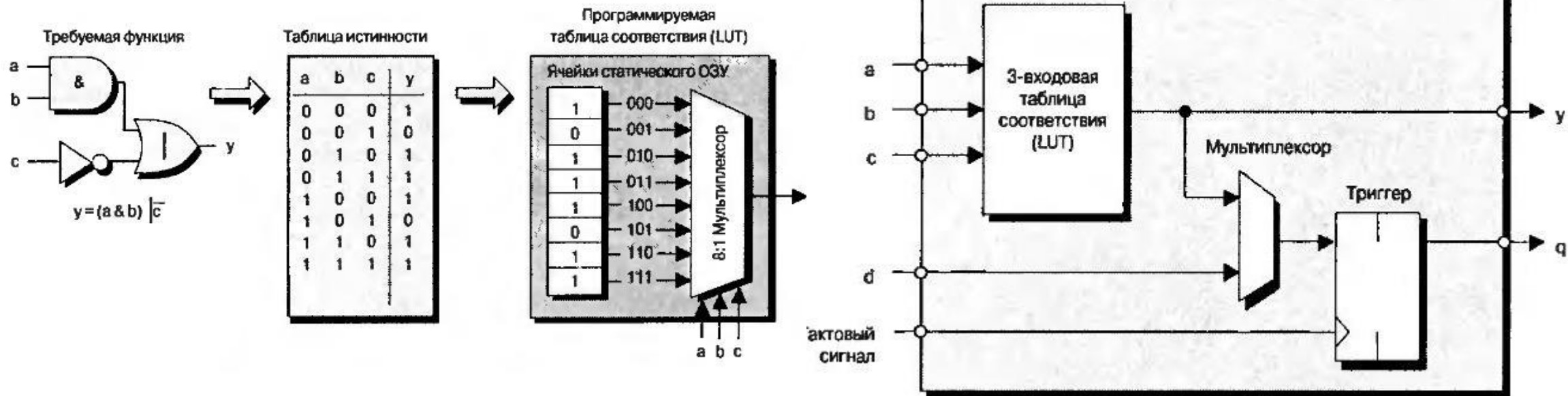


   

 

 


 

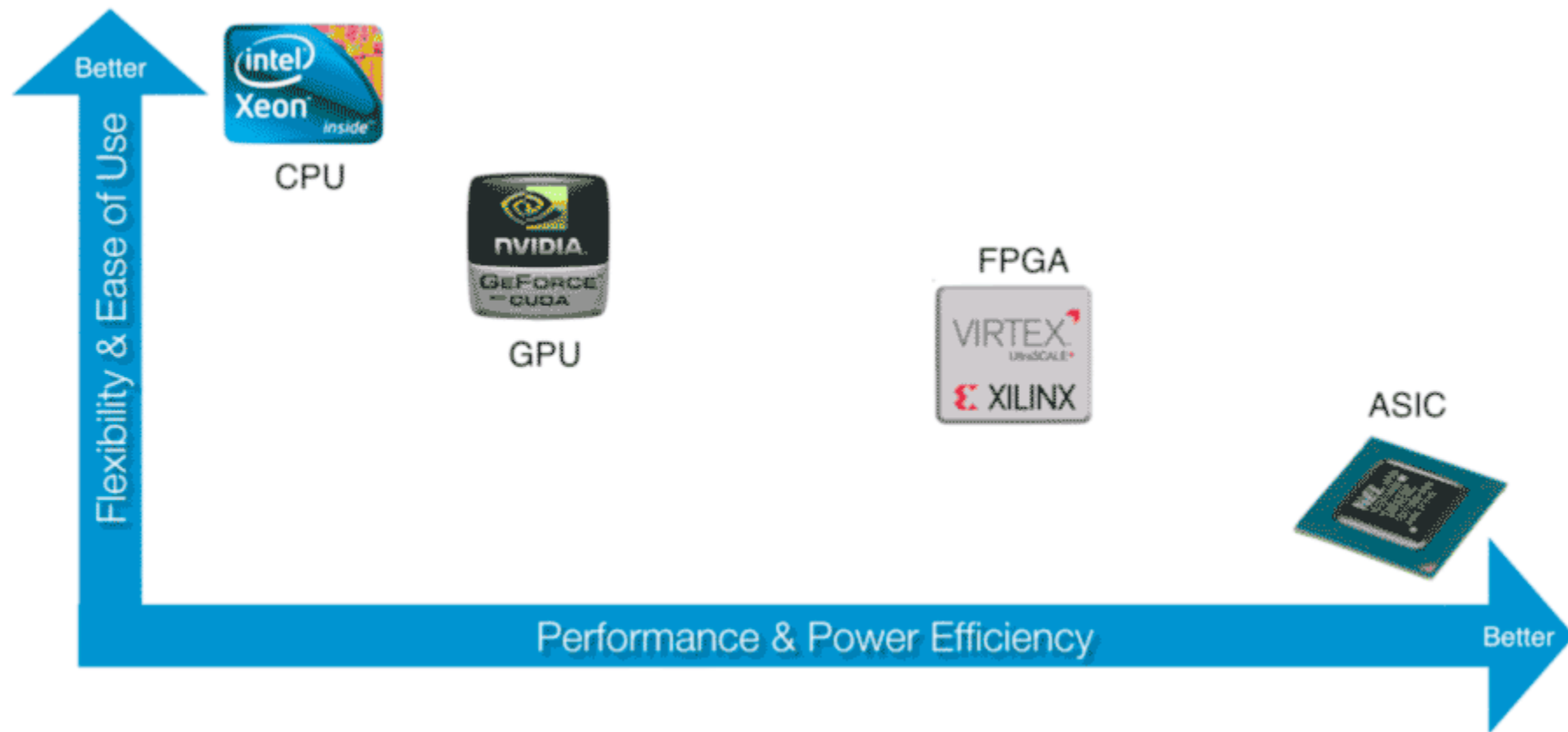


Преимущества системы на кристалле:

 - повышение степени интеграции приводит к миниатюризации устройств, как правило, система состоит из одной СБИС и ограниченного набора дискретных компонент, которые по технологическим причинам не могут быть интегрированы внутрь ИС.
- снижение потребляемой мощности.
- повышение надежности. Объединение нескольких компонент в одной ИС позволяет существенно уменьшить число паяных соединений.



Дискретные
элементы

Электронные
компоненты

 

Жесткая логика

IP-Блоки (Intellectual Property):

- микропроцессор,
- модули ЦОС,
- ОЗУ,
- ПЗУ,
- интерфейсные модули.



2019.2



Copyright 1986-2019 Xilinx, Inc.
All Rights Reserved.

project_1 - [D:/git/project_1/project_1.xpr] - Vivado 2019.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access write_bitstream Complete ✓ Default Layout

Flow Navigator PROJECT MANAGER - project_1

PROJECT MANAGER

- Settings
- Add Sources
- Language Templates
- IP Catalog

IP INTEGRATOR

- Create Block Design
- Open Block Design
- Generate Block Design

SIMULATION

- Run Simulation

RTL ANALYSIS

- Open Elaborated Design

SYNTHESIS

- Run Synthesis
- Open Synthesized Design

IMPLEMENTATION

- Run Implementation
- Open Implemented Design

PROGRAM AND DEBUG

- Generate Bitstream
- Open Hardware Manager
 - Open Target
 - Program Device
 - Add Configuration Memory Device

Sources

- Design Sources (1)
 - basic (basic.v)
- Constraints (1)
 - constrs_1 (1)
 - constr.xdc
- Simulation Sources (1)
 - sim_1 (1)
- Utility Sources

Hierarchy Libraries Compile Order

Properties

constr.xdc

- Enabled
- Location: D:/git/project_1/project_1.srcs/constrs_1/new
- Type: XDC
- Size: 19.3 KB
- Modified: Today at 23:23:38 PM
- Copied to: D:/git/project_1/project_1.srcs/constrs_1/new

General Properties

Tcl Console Messages Log Reports Design Runs

Name	Constraints	Status	WNS	TNS	WHS	THS	TPWS	Total Power	Failed Routes	LUT	FF	BRAM	URAM	DSP	Start	Elapsed	Run Strategy
synth_1	constrs_1	synth_design Complete!								8	0	0.0	0	0	8/31/21, 11:24 PM	00:00:36	Vivado Synthesis Defaults
impl_1	constrs_1	write_bitstream Complete!	NA	NA	NA	NA	NA	10.302	0	8	0	0.0	0	0	8/31/21, 11:25 PM	00:02:26	Vivado Implementation Defaults

Project Summary basic.v constr.xdc

D:/git/project_1/project_1.srcs/sources_1/new/basic.v

```
//  
// Create Date: 08/31/2021 11:15:35 PM  
// Design Name:  
// Module Name: basic  
// Project Name:  
// Target Devices:  
// Tool Versions:  
// Description:  
//  
// Dependencies:  
//  
// Revision:  
// Revision 0.01 - File Created  
// Additional Comments:  
//  
/////////////////////////////////////  
  
module basic (  
    input [15:0] SW,  
    output [15:0] LED  
);  
  
assign LED[0] = SW[0] & SW[1];  
assign LED[2] = SW[2] | SW[3];  
assign LED[4] = SW[4] ^ SW[5];  
assign LED[10:6] = ~SW[10:6];  
assign LED[13:11] = {SW[11], SW[12], SW[13]};  
assign LED[15:14] = {2{SW[14]}};
```


Процесс компиляции

▼ SYNTHESIS

▶ Run Synthesis

> Open Synthesized Design

Синтез и верификация Verilog кода

▼ IMPLEMENTATION

▶ Run Implementation

> Open Implemented Design

Имплементация (размещение на кристалле)

▼ PROGRAM AND DEBUG

⬇ Generate Bitstream


> Open Hardware Manager

Bitstream (генерация прошивки)

Verilog HDL

module

endmodule

 

```
module top
```

```
endmodule
```




A diagram of a module box. It is a light gray rectangle with rounded corners and a thin black border. The word "top" is written in black text in the top right corner of the box.

top

```
module top ();
```


```
endmodule
```

 

```
module top (  
    input  
    input  
    input  
    output  
);
```

a,
b,
clk,
q


```
endmodule
```

 


```
module top (  
    input    a,  
    input    b,  
    input    clk,  
    output    q  
);
```

```
    wire c;
```


```
endmodule
```

 
 
```
module top (  
    input    a,  
    input    b,  
    input    clk,  
    output   q  
);  
  
wire c;  
  
assign c = a;  
  
endmodule
```



 
```
module top (  
    input    a,  
    input    b,  
    input    clk,  
    output   q  
);  
  
wire c;  
  
assign c = a & b;  
  
endmodule
```



```
module fulladder (a, b, cin, s, cout);
```

```
    input  a, b, cin;
```

```
    output s, cout;
```

```
    wire p, g;
```


```
    assign p = a ^ b;
```

```
    assign g = a & b;
```


```
    assign s = p ^ cin;
```

```
    assign cout = g |(p & cin);
```

```
endmodule
```

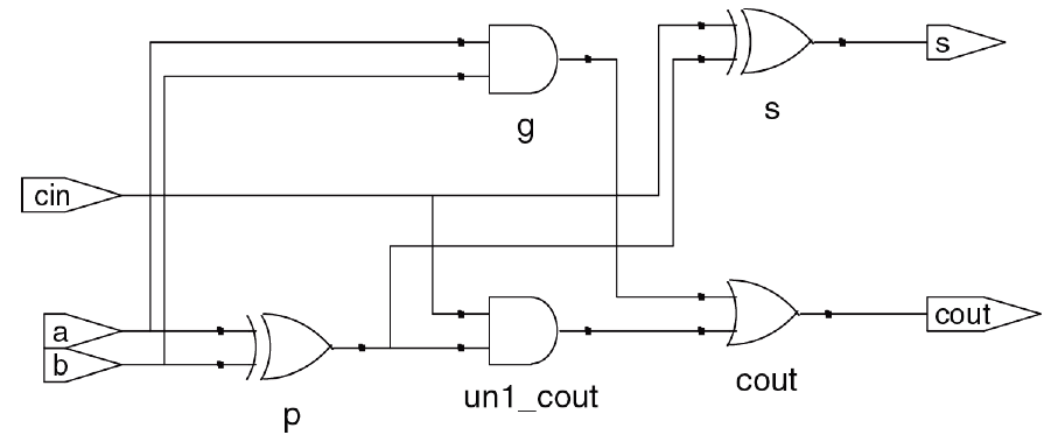

 
```
module top (  
    input    a,  
    input    b,  
    input    clk,  
    output    q  
);  
  
wire c;  
  
assign c = a & b;  
  
endmodule
```




```
module top (  
    input    a,  
    input    b,  
    input    clk,  
    output    q  
);
```

```
    wire c;  
    reg t;  
    assign c = a & b;
```


```
endmodule
```

 

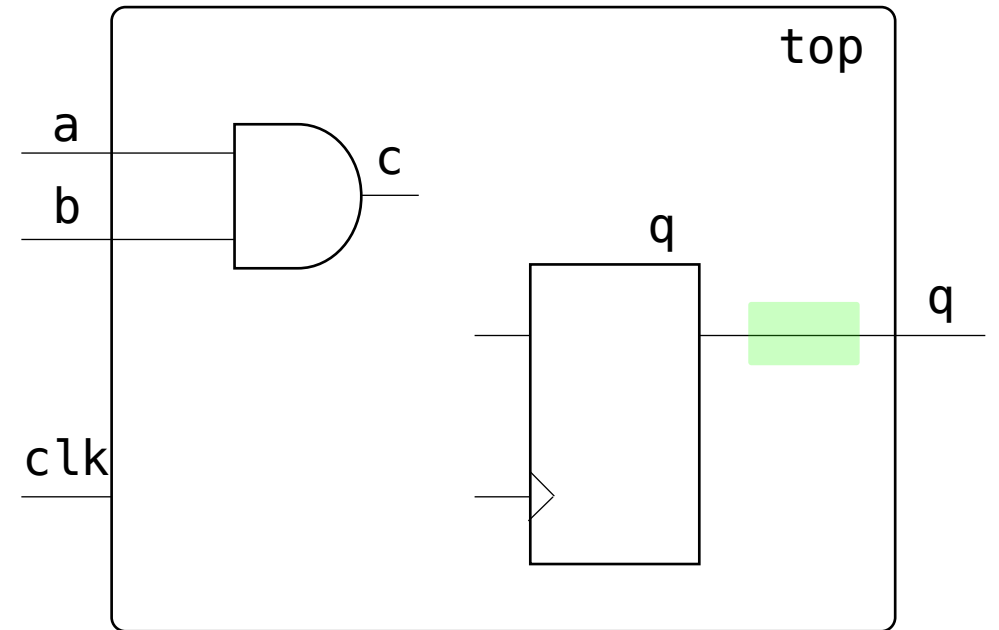
```
module top (  
    input    a,  
    input    b,  
    input    clk,  
    output reg q  
);  
  
wire c;  
  
assign c = a & b;  
  
endmodule
```



 
```
module top (  
    input      a,  
    input      b,  
    input      clk,  
    output reg  q  
);  
  
wire c;  
  
assign c = a & b;  
  
always @ (  
  
endmodule
```



 
```
module top (  
    input      a,  
    input      b,  
    input      clk,  
    output reg  q  
);  
  
wire c;  
  
assign c = a & b;  
  
always @ (posedge clk)  
  
endmodule
```



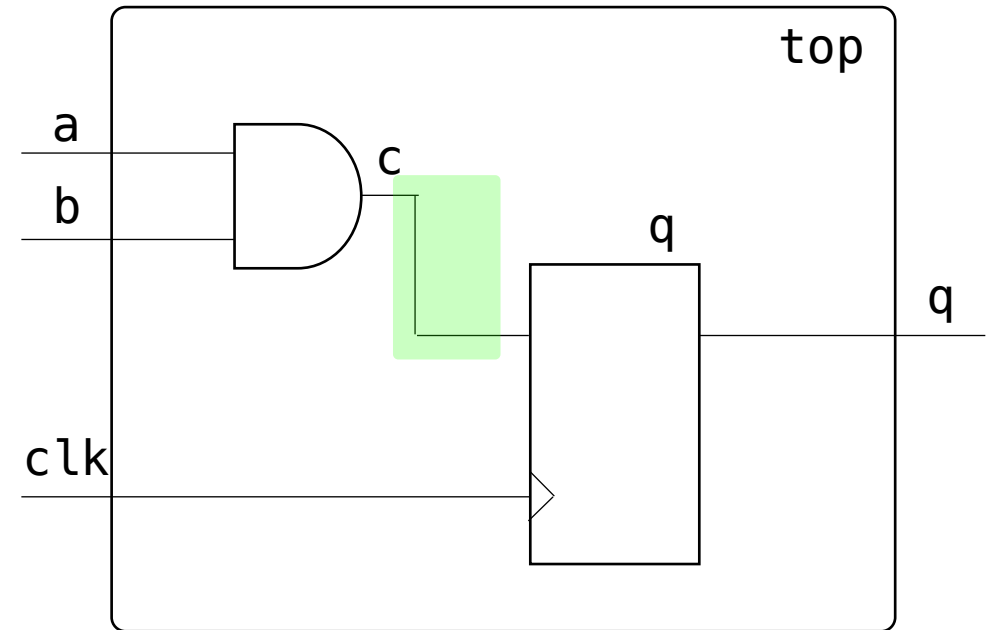
```
module top (  
    input    a,  
    input    b,  
    input    clk,  
    output reg q  
);  
  
wire c;  
  
assign c = a & b;  
  
always @ (posedge clk)  
    q <= c;  
  
endmodule
```



 
```
module top (  
    input      a,  
    input      b,  
    input      clk,  
    output reg  q  
);  
  
wire c;  
  
assign c = a & b;  
  
always @ (posedge clk)  
    q <= c;  
  
endmodule
```



 
```
module top (  
    input      a,  
    input      b,  
    input      clk,  
    output reg  q  
);  
  
wire c;  
  
always @ (posedge clk)  
    q <= c;  
  
assign c = a & b;  
  
endmodule
```



```
module top (  
    input      a,  
    input      b,  
    input      clk,  
    output reg  q  
);
```

```
always @ (posedge clk)  
    q <= a & b;
```

```
endmodule
```

 


Комбинационная логика

```
module dut (  
    input  a, b, c,  
    output y  
);
```


```
assign y = a & ~b & ~c | a & ~b & c | a & ~b & c;
```

```
endmodule
```

 


Иерархия модулей в Verilog
 
```
module and_3 (  
    input a, b, c,  
    output y  
);  
  
assign y = a & b & c;  
  
endmodule
```


 
```
module inv (  
    input a  
    output y  
);  
  
assign y = ~a;  
  
endmodule
```



Иерархия модулей в Verilog


```
module dut (  
    input  a, b, c,  
    output y  
);
```

```
wire n1;
```

```
and_3 andgate (  
    .a(a),  
    .b(b),  
    .c(c),  
    .y(n1)  
);
```

```
inv inverter (  
    .a(n1),  
    .y(y)  
);
```


```
endmodule
```

 

- Имя подключаемого модуля (**and_3**, **inv**)
- Название примитива. Например, нам может понадобиться 3 копии модуля **and_3**. Тогда мы сможем подключить 3 экземпляра модуля **and_3**, используя различные наименования для прототипов (**andgate_1**, **andgate_2** ...)
- Символ точка, перед наименованием порта отсылает к реальному порту подключаемого модуля (у модуля **inverter**, порты именуются **a**, **y**). В скобках обозначается куда будут подключаться сигналы в *top*-модуле

Тернарный оператор

 
```
module ternary (  
    input  [3:0] d0, d1,  
    input      s,  
    output [3:0] y  
);  
  
assign y = s ? d1 : d0;  
  
endmodule
```



? : данный оператор называется тернарным, т.к. в нем используется **3** входных значения: `s`, `d1`, `d0`.


D-триггер
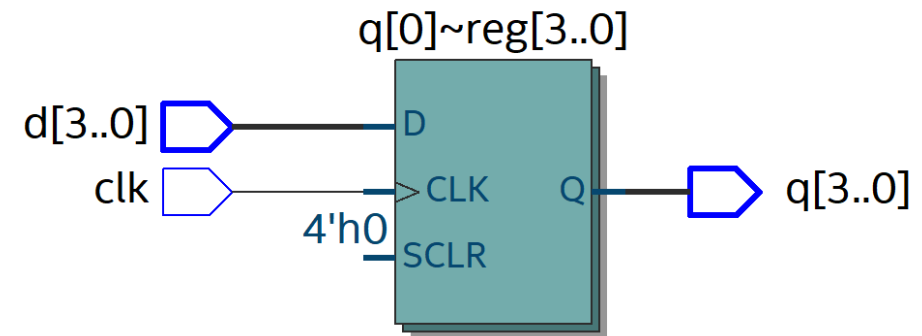
```
module flop (  
    input  
    input [3:0] d,  
    output reg [3:0] q  
);  
  
always @ (posedge clk)  
    q <= d;  
  
endmodule
```




D-триггер, с синхронным сбросом


 
```
module flopr (  
    input          clk,  
    input          reset,  
    input [3:0]    d,  
    output reg [3:0] q  
);  
  
always @ (posedge clk)  
    if (reset)      q <= 4'b0;  
    else            q <= d;  
  
endmodule
```



D-триггер, с асинхронным сбросом

 
```
module flopr (  
    input          clk,  
    input          reset,  
    input [3:0]    d,  
    output reg [3:0] q  
);  
  
always @ (posedge clk or posedge reset)  
    if (reset)        q <= 4'b0;  
    else                q <= d;  
  
endmodule
```



  



CASE
 
```
module mux (  
    input [3:0] d0, d1, d2, d3,  
    input [1:0] s,  
    output reg [3:0] y  
);  
  
always @ (*) begin  
    case (s)  
        2'b00: y = d0;  
        2'b01: y = d1;  
        2'b10: y = d2;  
        2'b11: y = d3;  
    endcase  
end  
  
endmodule
```





Неблокирующее присваивание
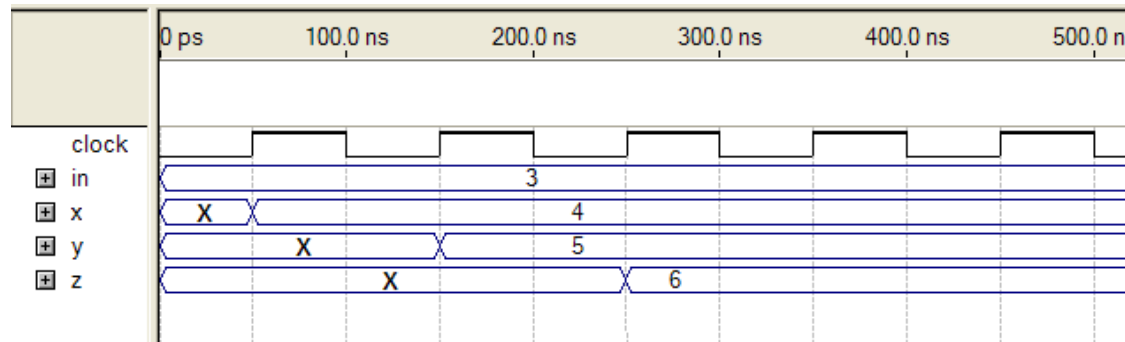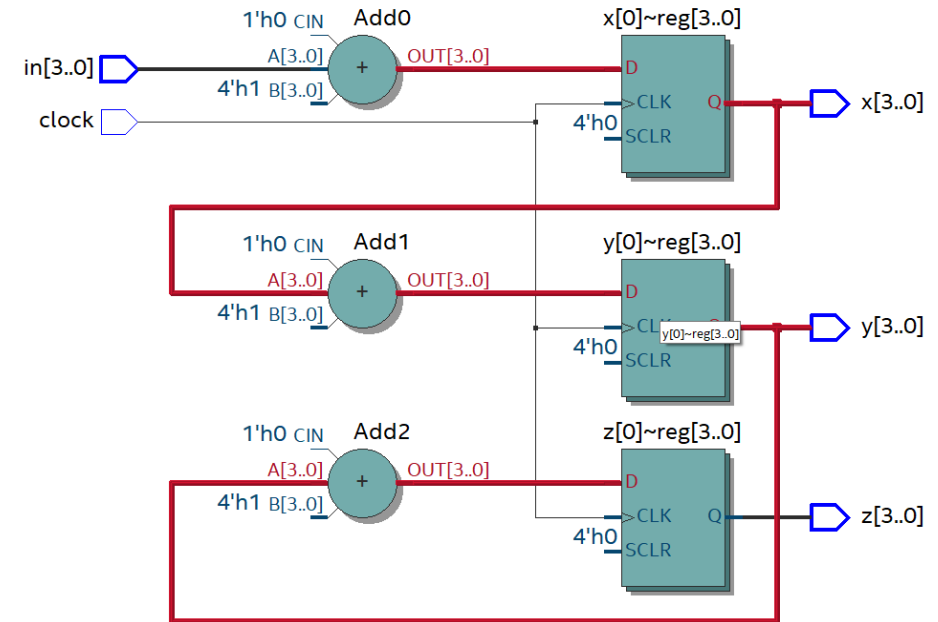
```
module test (  
    input                clock,  
    input [3:0]          in,  
    output reg [3:0]     x,  
    output reg [3:0]     y,  
    output reg [3:0]     z  
);  
  
always @ (posedge clock) begin  
    x <= in + 1;  
    y <= x + 1;  
    z <= y + 1;  
end  
  
endmodule
```




Блокирующее присваивание
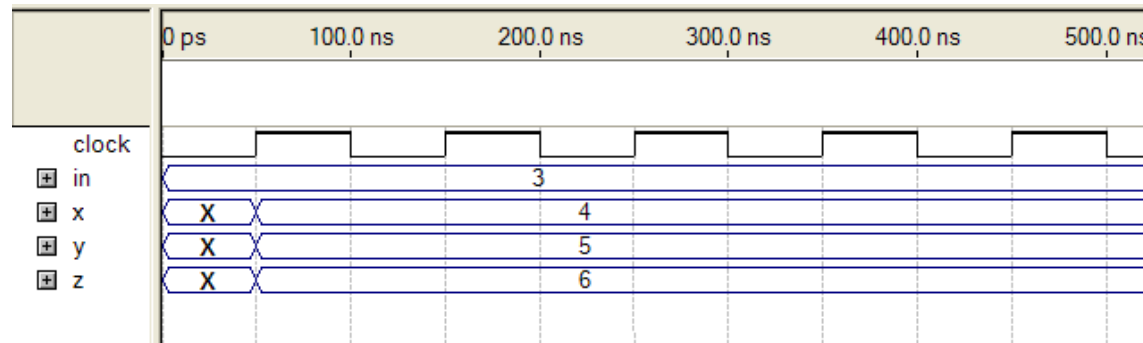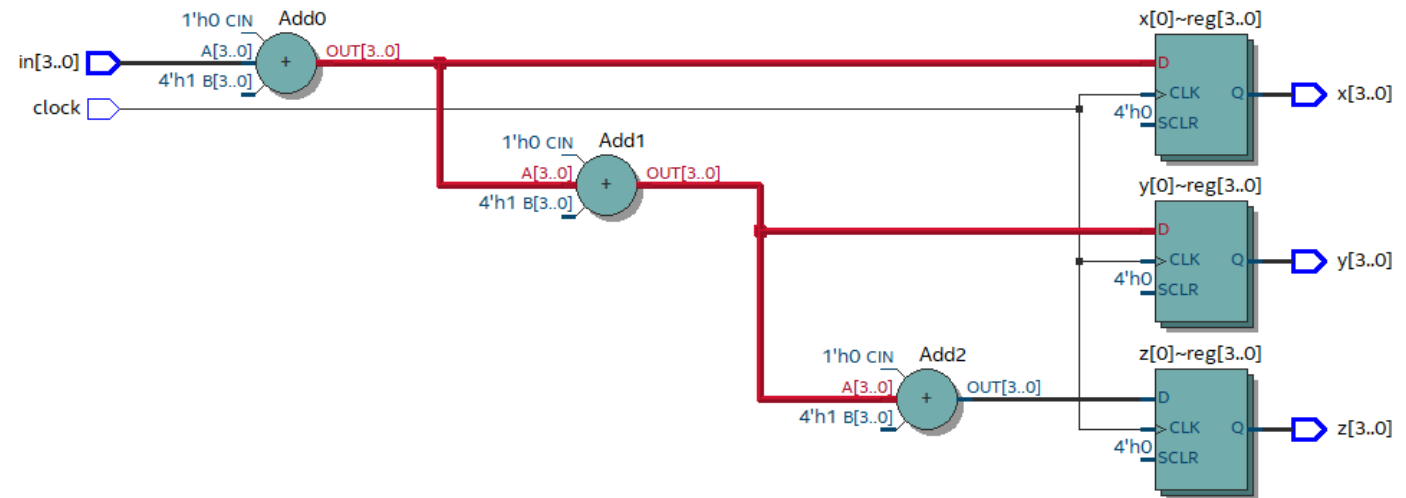
```
module test (  
    input          clock,  
    input [3:0]    in,  
    output reg [3:0] x,  
    output reg [3:0] y,  
    output reg [3:0] z  
);  
  
always @ (posedge clock) begin  
    x = in + 1;  
    y = x + 1;  
    z = y + 1;  
end  
  
endmodule
```




Тестовое окружение

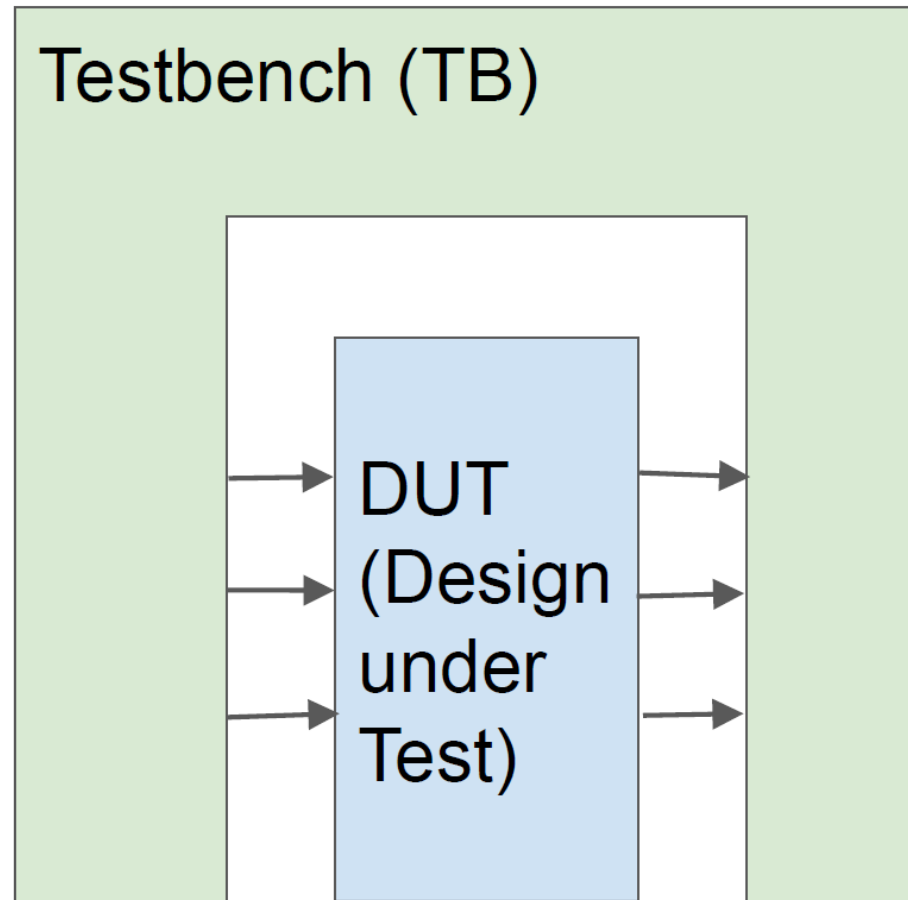

```
module my_module (  
    input a, b, c,  
    output y  
);
```

```
assign y = a & ~b & ~c | a & ~b & c | a & ~b & c;
```

```
endmodule
```

 


```
`timescale 1ns / 1ps


module testbench ();



    reg    a, b, c;
    wire   y;

    my_module dut (a, b, c, y);



    initial begin
        a = 0; b = 0; c = 0; #10;
        if (y === 1)
            $display("Good");
        else
            $display("Bad");
        c = 1; #10;
    end

endmodule
```


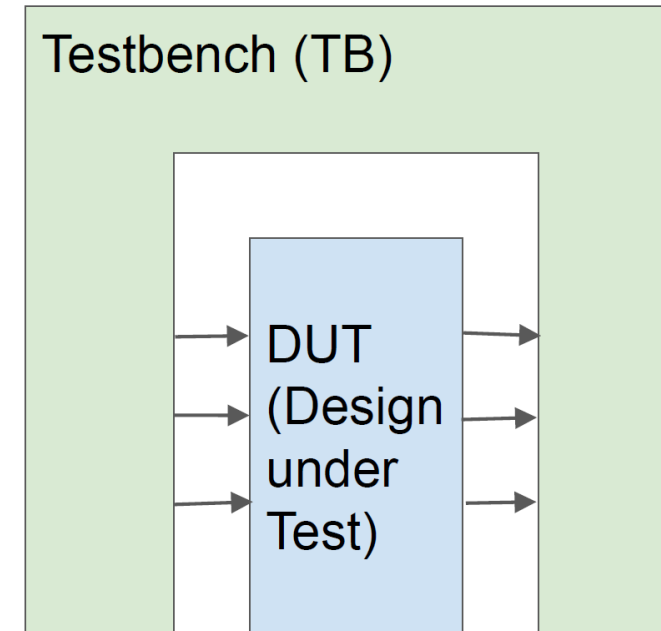


  

Critical Path

  

Critical Path

  

Short Path

